
Application note

Connecting the WindSensor P2546D-OPR

The WindSensor P2546D-OPR Cup Anemometer has an open collector transistor output with the frequency proportional to the wind speed. A control circuit inside the P2546D-OPR switches the open collector output between open state (floating) and closed state (grounded) when the cup rotor assembly is rotated by the wind.

The P2546D-OPR must be connected to a counter/frequency input on a datalogger using a pull-up (or pull-down) resistor to provide a well-defined signal when the open collector output is floating. The pull-up resistor must be connected to the supply voltage or if available an excitation voltage on the datalogger. A recommended value of the pull-up resistor is 10 K Ω . Figure 1 shows an example of connecting the P2546D-OPR to a datalogger using an external pull-up resistor. Please refer to the datalogger documentation for specific details on how to connect the P2546D-OPR to the datalogger.

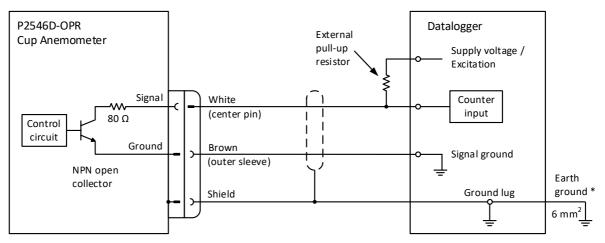

* Connect the datalogger's ground lug to earth ground. Connect the ground lug to the nearest point at a met. tower or turbine structure, and trim the wire to the shortest possible length. Maintain the integrity and continuity of the shield connection in all intermediate junction boxes used.



Dataloggers with internal pull-up or pull-down resistors may be connected to the P2546D-OPR without using an external resistor. Adding an external resistor is however recommended to reduce noise sensitivity, when using dataloggers with high resistance pull-up or pull-down resistors. When e.g. using a Campbell CR1000 datalogger with 100 k Ω pull-up resistors on the P-terminals and 100 k Ω pull-down resistors on the C-terminals, adding an external 12 k Ω resistor is recommended. Figure 2 show examples of connecting the P2546D-OPR open collector output to dataloggers with internal pull-up or pull-down resistors.

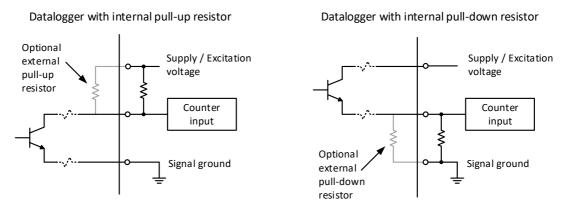


Figure 2: P2546D-OPR connection using an internal pull-up (left) or pull-down (right) resistor.



WINDSENSOR reducing uncertainty

Using a pull-up resistor will provide a high level output voltage with the output transistor in open state (transistor turned off and output tied to supply voltage / excitation) and a low level output voltage with the output transistor in closed state (transistor turned on and output tied to ground). Using a pull-down resistor provides the opposite output level with a low level in the open state and a high level in the closed state. Figure 3 shows the waveform for one revolution of the cup anemometer rotor.

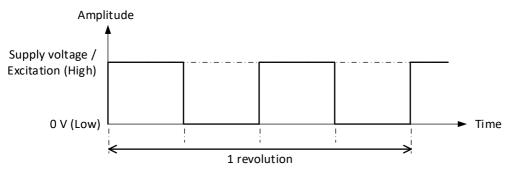


Figure 3: Datalogger counter input waveform.

